



## 1.0 Design Specifications

Inputs	Outputs #1
VinMin=8.0	Vout1=74
VinMax=12.0	Iout1=0.030


## 2.0 Design Description

This design drives 20 white LEDs in a single string at 30mA to light a vanity mirror. The circuit boosts the input voltage in order to keep 20 LEDs in a single series string. This ensures that the same current flows through each device which results in equal brightness. The resistor Rset is used to set the load current in the following manner:  $R_{set} = 1.25V / \text{Load current}$ . To drive the string of LEDs at 30mA, a 41.2ohm resistor can be used for Rset.

The design features the LM5000 which is a monolithic integrated circuit specifically designed and optimized for flyback, boost or forward power converter applications. The internal power switch is rated for a maximum of 80V, with a current

limit set to 2A. Protecting the power switch are current limit and thermal shutdown circuits. The current mode control scheme provides excellent rejection of line transients and cycle-by-cycle current limiting. An external compensation pin and the built-in slope compensation allow the user to optimize the frequency compensation. Other distinctive features include softstart to reduce stresses during start-up and an external shutdown pin for remote ON/OFF control. There are two operating frequency ranges available. The LM5000-3 is pin selectable for either 300kHz (FS Grounded) or 700kHz (FS Open). The LM5000-6 is pin selectable for either 600kHz (FS Grounded) or 1.3MHz (FS Open). The device is available in a low profile 16-lead TSSOP package or a thermally enhanced 16-lead LLP package.

## 3.0 Schematic

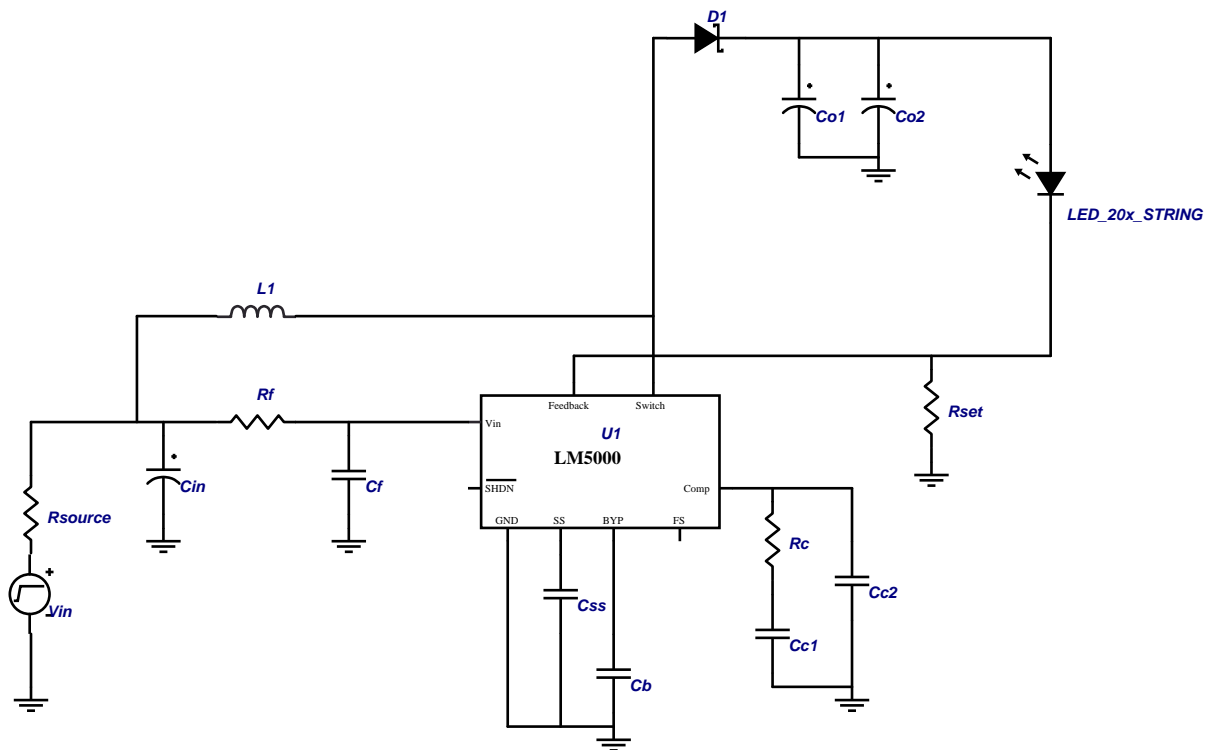


689758\_776\_0

FIGURE 1. Example Schematic Showing Connection for all Components.

## 4.0 Bill Of Materials


Part	Manufacturer	Part#	Attributes
Cb	Vishay	VJ1206Y103KXXAT	100n F
Cc1	Vishay	VJ1206Y683KXXAT	68n F
Cf	Vishay	VJ1203Y474KXXAT	470n F
Cin	TDK	C3225X5R1C106M	NumCaps=1, 10u F
Co1	TDK	C4532X5R1A225M	2.2u F
Co2	TDK	C4532X5R1A225M	2.2u F
Css	Vishay	VJ1206Y103KXXAT	10n F
D1	ONSEMI	MBRS190T3	0.75 V
L1	TDK	SLF12565T-101M1R6	100n H, 0.1476 Ohms
Rc	Vishay	CRCW12062492F	24.9k Ohms
Rf	Vishay	CRCW1206100J	10 Ohms
Rset	Vishay	CRCW1206xxxJ	
U1	National Semiconductor	LM5000	

# 5.0 Layout

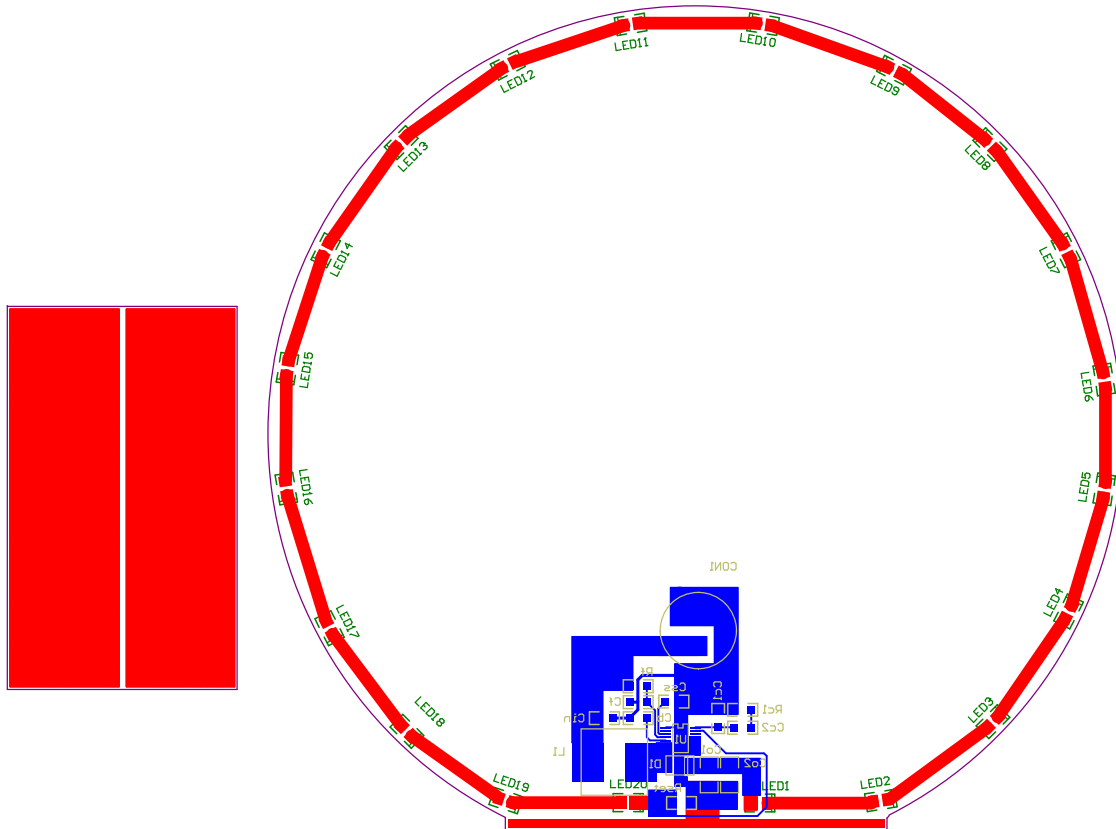

PADC\_LED001\_lo\_1

FIGURE 2. Board's Bottom View

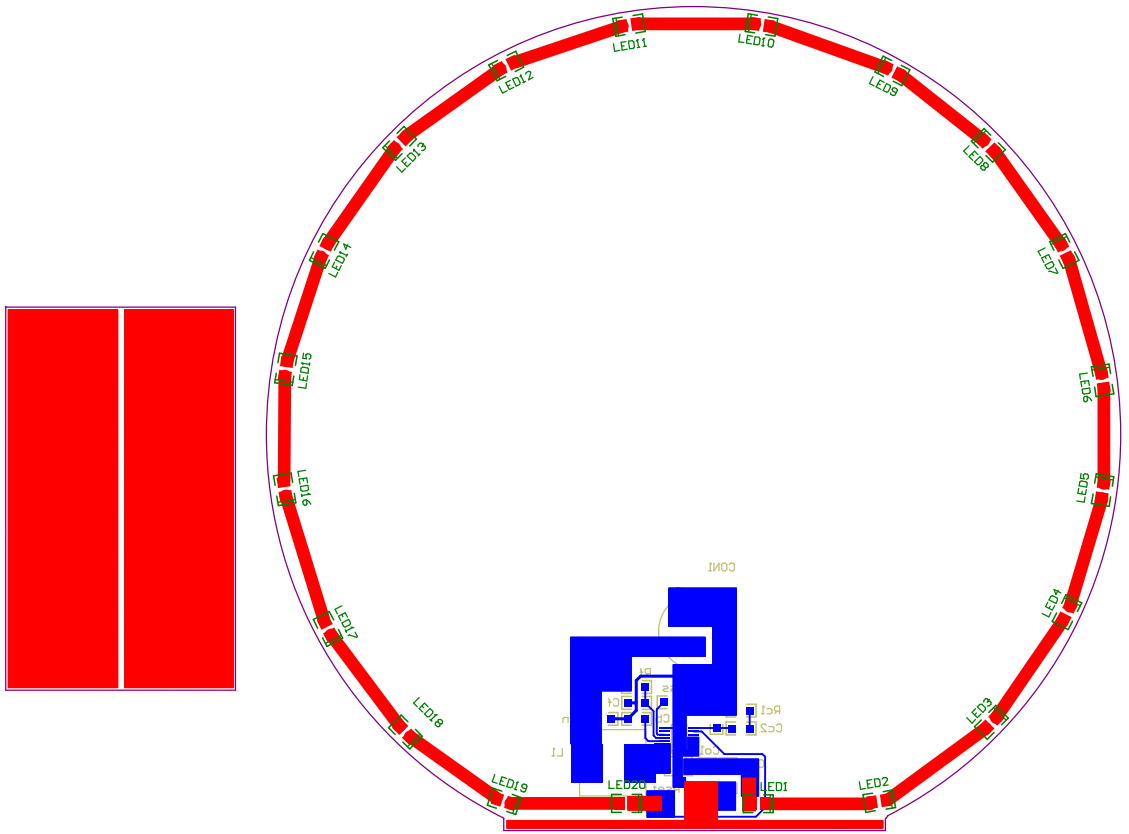

PADC\_LED001\_1o\_2

FIGURE 3. Board's Top View

# Notes

## Notes

National Semiconductor's design tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Reference designs are created using National's published specifications as well as the published specifications of other device manufacturers. While National does update this information periodically, this information may not be current at the time the reference design is built. National and/or its licensors do not warrant the accuracy or completeness of the specifications or any information contained therein. National and/or its licensors do not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. National and/or its licensors do not warrant that the designs are production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at [www.national.com](http://www.national.com).

### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which,
  - (a) are intended for surgical implant into the body, or
  - (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

### BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



**National Semiconductor Americas Customer Support Center**  
 Email: [new.feedback@nsc.com](mailto:new.feedback@nsc.com)  
 Tel: 1-800-272-9959

**National Semiconductor Europe Customer Support Center**  
 Fax: +49 (0) 180-530-85-86  
 Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)  
 Deutsch Tel: +49 (0) 69 9508 6208  
 English Tel: +49 (0) 870 24 0 2171  
 Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia Pacific Customer Support Center**  
 Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan Customer Support Center**  
 Fax: 81-3-5639-7507  
 Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)  
 Tel: 81-3-5639-7560